

# **EM430F6137RF900 Reference Design Guide**

Miguel Morales

MSP430, LP-RF

## **ABSTRACT**

This document explains the theory behind and recommended practices to layout the EM430F6137RF900's RF filter-balun. It also describes tips and tricks for the EM430F6137RF900, including steps to modify the RF-front end to operate at 315 MHz or 433 MHz, necessary additions for BSL communication, recommendations for achieving ETSI compliance, and how to debug the EM430F6137RF900 board using Spy-Bi-Wire mode.

## **Contents**

1	Impedance Matching and Filter Design Principles .....	2
2	EM430F6137RF900 RF Front End .....	4
3	EM430F6137RF900 Schematic Tips and Tricks .....	6
4	ETSI Compliance .....	7
5	References .....	7

## **List of Figures**

1	Typical Balun Circuit for 868/915 MHz .....	2
2	50-Ω Points in the Balun .....	3
3	Example Solder Paste, With and Without Vias (CC11xx) .....	4
4	RF Front End for 868 or 915 MHz .....	4
5	RF Front End for 315 MHz.....	5
6	RF Front End for 434 MHz.....	5
7	EM430 Front - SBW Communication.....	6

## **List of Tables**

1	Components for 868 or 915 MHz .....	4
2	Components for 315 MHz.....	5
3	Components for 434 MHz.....	6


## Glossary of Acronyms

BSL	Bootstrap loader
EM430	EM430F6137RF900 board
ML	Multi-layer
SBW	Spy-Bi-Wire
WW	Wire wound

## 1 Impedance Matching and Filter Design Principles

The CC430 has differential RF ports, RF\_P and RF\_N, that have an optimal impedance seen from the chip towards the antenna of  $Z = 86.5 + j43 \Omega$  at 868/915 MHz and  $116 + j41 \Omega$  at 433 MHz. [6] The impedance of the selected antenna port is  $50 \Omega$ . Therefore, it is important to ensure proper impedance matching between the radio and the antenna through the use of a circuit network that translates a balanced signal from the CC430 to a  $50\text{-}\Omega$  unbalanced antenna load. This circuit is called a balun.

A typical application circuit for 868/915 MHz, including the balun, is shown in Figure 1.

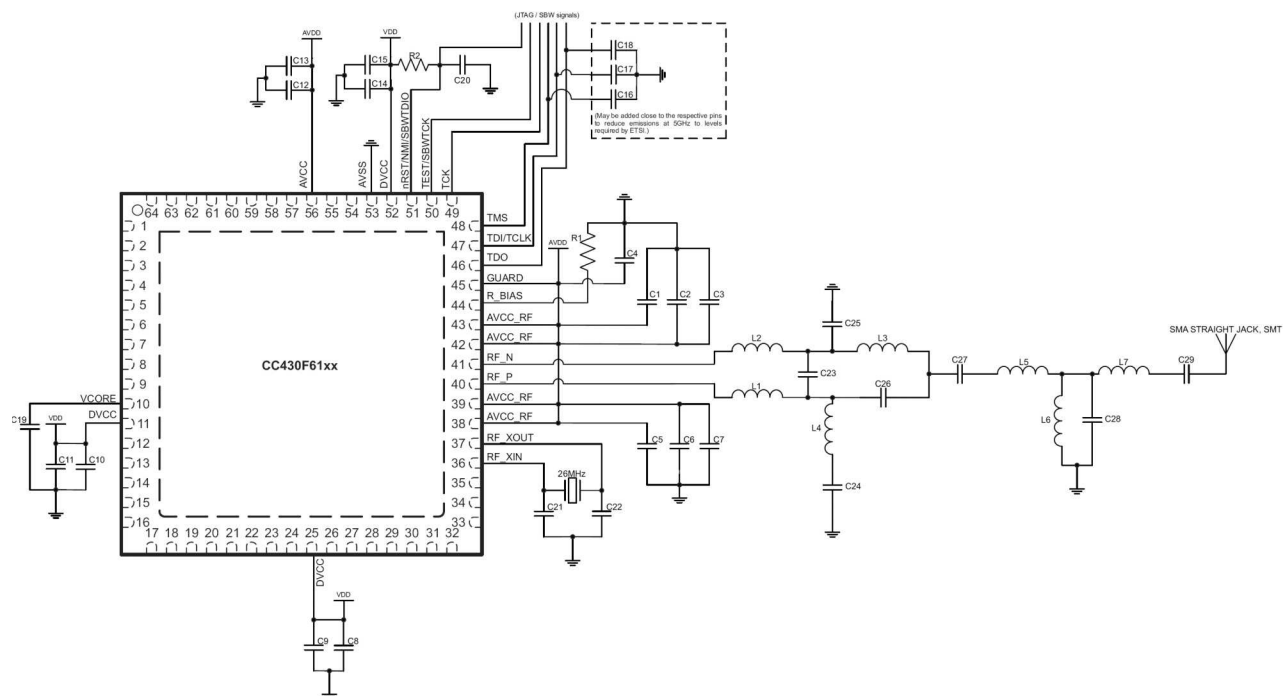

**Figure 1. Typical Balun Circuit for 868/915 MHz**

In transmit (TX) mode, the balun has two purposes:

- Provide optimum matching for the lowest possible current consumption and highest possible output power
- Fulfill regulatory harmonic and spurious emissions regulations

In receive (RX) mode, the balun has a single purpose:

- Provide optimum matching for the best possible sensitivity

The balun can be functionally divided into its different parts:

- Differential low-pass filter: L1, L2, C23
- Balun: C25, C26, L3, L4
- T-section band-pass filter: C27, C28, C29, L5, L6, L7
- DC block: C24


The recommended values of the balun components for different frequencies are documented in the EM430 reference design materials.

An ideal output signal from the CC430 in TX mode is a square wave signal at the RF\_P and RF\_N pins and a sine wave at the antenna port. To achieve this, the balun must successfully suppress the most prominent odd harmonics – the third and fifth – of the square wave. The lowest possible current consumption is achieved by having these odd harmonics reflected back towards the RF front-end with a high real part of the impedance. The easiest way to do this is through the use of the differential low-pass filter.

Following the low-pass filter is the balun that matches the impedance of the output to the 50-Ω node. The filter is designed to shift the output signal in phase by  $\pm 90^\circ$  through the use of a low-pass and a high-pass filter. To achieve the best amplitude and phase balance in the balun, the layout trace from the single-ended port to each of the RF pins should be as equal in length and as symmetrical as possible. Any unbalance in the balun design causes high second and fourth harmonic levels, reduced output power at the single-ended side of the balun, higher transmit current consumption, and reduced sensitivity.

The filter that follows the balun is recommended to be T-type filter, rather than a Pi-type, to reduce the radiated emissions through shunt capacitors.

In the case of the EM430 reference design, the filter is a band-pass filter, and it is dimensioned to have a 50-Ω impedance at both sides so it can easily be removed or redesigned to fulfill any special requirements (see [Figure 2](#)).

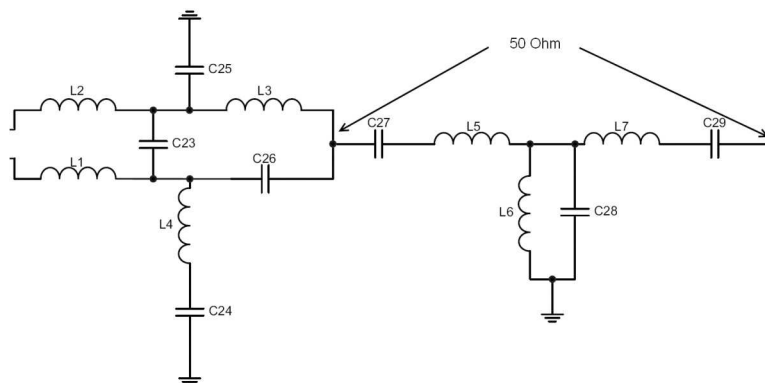

**Figure 2. 50-Ω Points in the Balun**

### 1.1 Filter and Balun Layout Best Practices

The following key considerations should be taken into account during layout:

- The traces for the RF layout should be symmetrical.
- A solid ground-plane should be implemented beneath the RF circuitry.
- It is recommended that the distance between layer 1, with the RF circuitry, and ground is 410 μm. Changing the thickness of the board changes the inductance of the vias which, in series with the decoupling capacitors, could negatively affect the performance. The EM430F6137RF900 PCB uses 4-layer technique with the distance between the TOP (RF circuitry) and GND layers being 410 μm.
- Shorter or longer trace lengths may degrade the performance, because they will influence the impedance of the traces in the balun.
- The design should be implemented on an FR4 substrate. Changing the substrate will affect the impedance of the PCB traces.
- Decoupling capacitors C1 to C15 should be used and should be placed as close to the pins as possible. [1] Vias should be placed close to all decoupling capacitors to ensure a good connection to the solid ground plane below.
- 0402 components are used for the CC430 reference design. Changing to 0603 will change the parasitic values of the components and may require a different solution.
- Components from different vendors have slightly different performance. Inductors and capacitors from Murata (the LQW15 and GRM15 series) are used in the CC430F613x/F513x reference design.

- Multi-layer (ML) type inductors are used in the CC430F613x/F513x reference design. A slightly higher output power and reduction of harmonic emissions can be achieved by replacing the ML type of inductors with wire wound (WW) inductors. ML inductors were chosen for the reference design due to tradeoffs in cost.

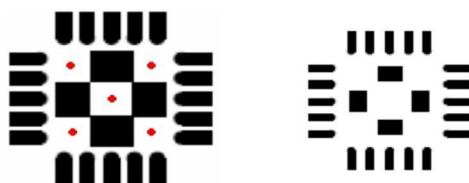


Figure 3. Example Solder Paste, With and Without Vias (CC11xx)

## 2 EM430F6137RF900 RF Front End

The RF front-end is a balun circuit required to match the impedance of the differential CC430 outputs to a 50-Ω load, such as the monopole SMA antenna provided with the EM430 kit, an RF signal generator, or a spectrum analyzer. The EM430 comes populated with the RF front end intended to operate within the 868- or 915-MHz frequency bands (see Figure 4 and Table 1).

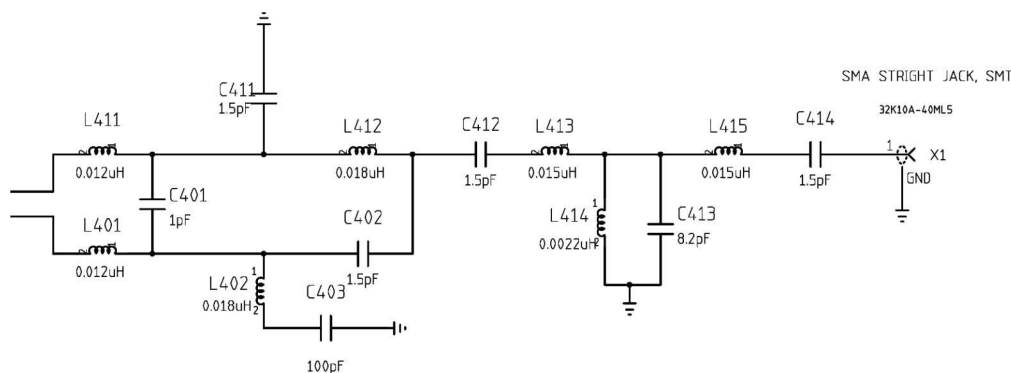


Figure 4. RF Front End for 868 or 915 MHz

Table 1. Components for 868 or 915 MHz

Qty	Mfg	Part No	Value	Description	Schematic Reference
2	Murata	LQW15AN12NJ00	12nH	INDUCTOR,SMT, 0402,+/-5%,500mA,250MHz	L411, L401
1	Murata	GJM1555C1H1R0CB01D	1pF	CAPACITOR, SMT, CERAMIC, 0402, 50V, +/-0.25pF, NP0	C401
4	Murata	GRM1555C1H1R5CZ01	1.5pF	CAPACITOR,S MT, CERAMIC, 0402, 50V, +/-0.25pF, C0G(NP0)	C402,C411-C412,C414
1	Murata	GRM1555C1H101JZ01	100pF	CAPACITOR, SMT, CERAMIC, 0402, 50V, +/-0.25pF, C0G(NP0)	C403
2	Murata	LQW15AN18NJ00	18nH	INDUCTOR, SMT, 0402, +/-5%, 370mA, 250MHz	L402,L412
2	Murata	LQW15AN15NJ00	15nH	INDUCTOR, SMT, 0402, +/-5%, 460mA, 250MHz	L413,L415
	Murata	LQW15AN2N2C10	2.2nH	INDUCTOR, SMT, 0402, +/-0.2nH, 1000mA, 250MHz	L414
1	Murata	GRM1555C1H8R2CZ01	8.2pF	CAPACITOR, SMT, CERAMIC, 0402, 50V, +/-0.25pF, C0G(NP0)	C413
1	Nearson	S463 AM 915	50Ω	915 MHz antenna	

To successfully operate the EM board at the frequencies of 315 MHz and 433 MHz, the components of the balun circuit must be replaced. Section 2.1 and Section 2.2 describe the necessary component changes, and care should be taken to use either the exact components recommended in the bill-of-materials documents or components that have the same accuracy. Conveniently, the same board and RF layout may be re-used.

### 2.1 Changing the RF Front End For 315 MHz

The following excerpts from the respective schematics and BOM (see Figure 5 and Table 2) summarize the appropriate components and board modifications to change the CC430 EM into a 315-MHz board.

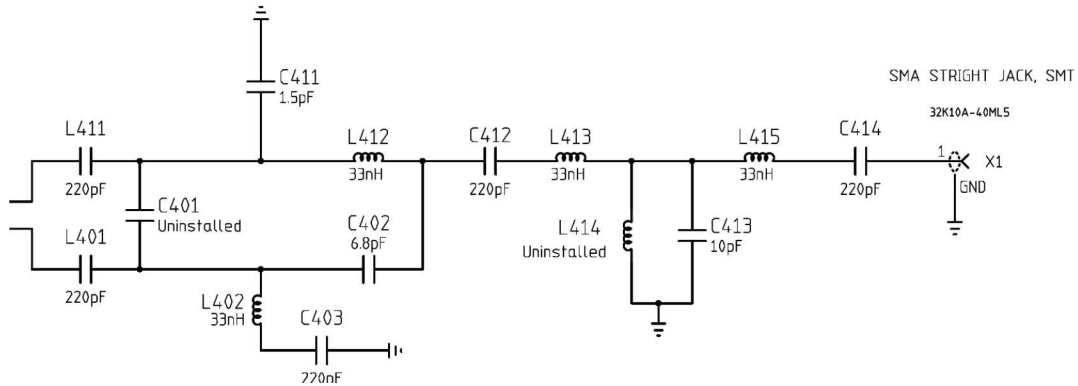


Figure 5. RF Front End for 315 MHz

Table 2. Components for 315 MHz

Qty	Mfg	Part No	Value	Description	Schematic Reference
1	Murata	LQP15MN2N2B02	Uninstalled	INDUCTOR, SMT, 0402, 2.2nH, +/-0.1nH, 220mA, 500MHz	L414
1	Murata	GRM1555C1H2R7BZ01	Uninstalled	CAPACITOR, SMT, CERAMIC, 0402, 2.7pF, 50V, +/-0.1pF, C0G	C401
5	Murata	GRM1555C1H221JA01	220pF	CAPACITOR, SMT, CERAMIC, 0402, 220pF, 50V, +/- 5%, C0G	C403, C412,
1	Murata	GRM1555C1H6R8CZ01	6.8pF	CAPACITOR, SMT, CERAMIC, 0402, 6.8pF, 50V, +/-0.25pF, C0G	C402
1	Murata	GRM1555C1H1R5CZ01	1.5pF	CAPACITOR, SMT, CERAMIC, 0402, 50V, +/-0.25pF, C0G(NP0)	C411
4	Murata	LQW15AN33NJ00	33nH	INDUCTOR, SMT, 0402, 33nH, +/-5%, 280mA, 500MHz	L402, L412-L413, L415
1	Murata	GRM1555C1H100JZ01	10pF	CAPACITOR, SMT, CERAMIC, 0402, 10pF, 50V, +/- 5%, C0G	C413
1	Nearson	L362AM-315R	50?	315 MHz antenna	

### 2.2 Changing the RF Front End For 434 MHz

The following excerpts from the respective schematics and BOM (see Figure 6 and Table 3) summarize the appropriate components and board modifications to change the CC430 EM into a 434-MHz board.

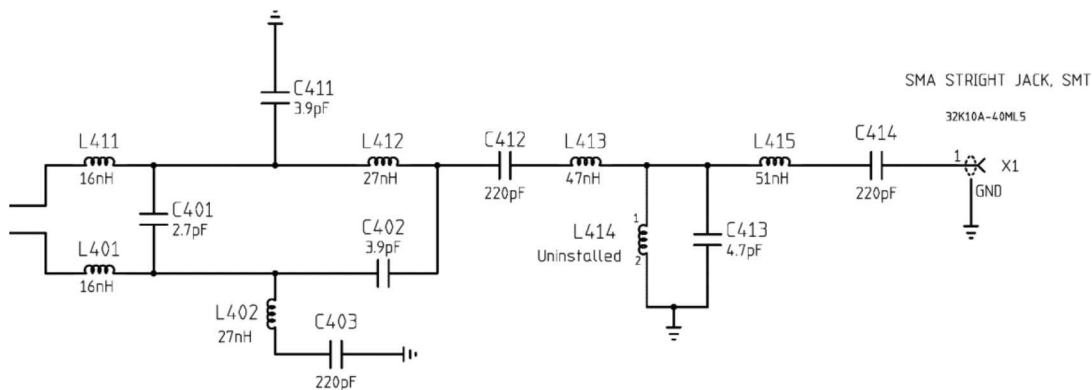


Figure 6. RF Front End for 434 MHz

**Table 3. Components for 434 MHz**

Qty	Mfg	Part No	Value	Description	Schematic Reference
1	Murata	LQP15MN2N2B02	Uninstalled	INDUCTOR, SMT, 0402, 2.2nH, +/-0.1nH, 220mA, 500MHz	L414
2	Murata	LQW15AN16NJ00	16nH	INDUCTOR, SMT, 0402, 16nH, +/-0.1nH, 130mA, 500MHz	L401, L411
2	Murata	LQW15AN27NJ00	27nH	INDUCTOR, SMT, 0402, 27nH, +/-5%, 280mA, 500MHz	L402, L412
2	Murata	GRM1555C1H3R9BZ01	3.9pF	CAPACITOR, SMT, CERAMIC, 0402, 3.9pF, 50V, +/-0.1pF, C0G	C402, C411
1	Murata	GRM1555C1H2R7BZ01	2.7pF	CAPACITOR, SMT, CERAMIC, 0402, 2.7pF, 50V, +/-0.1pF, C0G	C401
3	Murata	GRM1555C1H221JA01	220pF	CAPACITOR, SMT, CERAMIC, 0402, 220pF, 50V, +/- 5%, C0G	C403, C412, C414
1	Murata	LQW15AN51NJ00	51nH	INDUCTOR, SMT, 0402, 51nH, +/- 5%, 210mA, 100MHz	L415
1	Murata	LQW15AN47NJ00	4.7nH	INDUCTOR, SMT, 0402, 47nH, +/- 5%, 210mA, 100MHz	L413
1	Murata	GRM1555C1H4R7BZ01	4.7pF	CAPACITOR, SMT, CERAMIC, 0402, 4.7pF, 50V, +/-0.1pF, C0G	C413
1	Nearson	L362AM-434R	50?	434 MHz antenna	

### 3 EM430F6137RF900 Schematic Tips and Tricks

#### 3.1 Achieving Successful BSL Communication


To communicate in BSL mode, additional 0-Ω resistors must be populated on the EM430. When the EM430 is flipped over and the JTAG connector is pointed away at the top right of the board, two pairs of 0402 component pads are visible—one at the top left next to the back of CON10 and the other in the center of the board directly above CON1.

The pair of pads above CON1 is for R231 and R221 on the EM430 schematic. Both pads must be populated with 0-Ω resistors to communicate over BSL. The pair of pads next to COM10 at the top of the board is for R4 and R5 on the EM schematic. When supplying a voltage through the BSL connector populate R4 with a 0-Ω resistor. If supplying an external voltage, remove R4 and populate R5 with a 0-Ω resistor.

The resistors are marked on the silk screen.

#### 3.2 Communicating in Spy-Bi-Wire Mode

There is a row of six consecutive 0.1-in spacing jumpers populated at the top-center of the board. The two left-most jumpers in this set of six should be moved to connect to pins one and two on the header instead of pins five and six to successfully debug in Spy-Bi-Wire mode (see [Figure 7](#)).

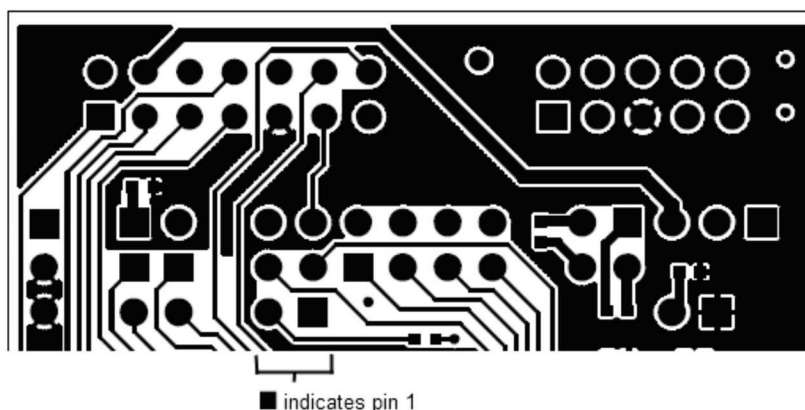
**Figure 7. EM430 Front - SBW Communication**

## 4 ETSI Compliance

Wire wound (WW) inductors perform better than multi layer at high frequencies because the self-resonant frequency is higher. By using WW instead of ML in the balun, it is possible to achieve better suppression of harmonic emission. ML inductors are less expensive than WW inductors. For an example of measurements based on the two different types of inductors, see *DN017 - CC11xx 868/915 MHz RF Matching*. [7]

### ETSI

ETSI EN 300 220 requires spurious emission above 1 GHz to be below -30 dBm. When using ML inductors, the highest PA setting that ensures compliance with ETSI is 0xC2. Using 0xC0, which is the CC430 PA setting resulting in maximum output power, results in a level of second harmonic which is at the ETSI limit. It is therefore recommended to use WW inductors in the balun to achieve highest possible output power when seeking compliance with ETSI EN 300 220.

### 4.1 Capacitors on TMS, TDI, and TDO Pins

For systems targeting compliance with the ETSI EN 300 220 in Europe, the receiver spurious radiations should not exceed -47 dBm for frequencies > 1000 MHz. To meet these requirements it is generally recommended to include 2-pF capacitors on the three JTAG pins TMS, TDI, and TDO. To check if the number of external components can be minimized, measurements should be performed with and without the capacitors mounted as the level of spurious emission is to some extent dependent on the PCB layout.

## 5 References

1. EM430F6137RF900\_Rev3\_2EB1\_schematic.pdf ([SLAC306](#))
2. EM430F6137RF900\_Rev3\_2EB1\_315\_schematic.pdf ([SLAC306](#))
3. EM430F6137RF900\_Rev3\_2EB1\_315\_BOM.pdf ([SLAC306](#))
4. EM430F6137RF900\_Rev3\_2EB1\_434\_schematic.pdf ([SLAC306](#))
5. EM430F6137RF900\_Rev3\_2EB1\_434\_BOM.pdf ([SLAC306](#))
6. CC430F613x/F513x data sheet ([SLAS554](#))
7. CC11xx 868/915 MHz RF Matching ([SWRA168](#))



## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

<b>Products</b>		<b>Applications</b>	
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>	Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>	Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>	Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>	Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>	Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>	Energy	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>	Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>	Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>	Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>	Space, Avionics & Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>	Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
		Wireless	<a href="http://www.ti.com/wireless-apps">www.ti.com/wireless-apps</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2010, Texas Instruments Incorporated